

# LAB 07

## LAB TASK

### TASK # 01

Design and Implement Octal to Binary Priority Encoder on Bread Board using 74148 IC.

### TASK # 02

Design and Implement Decimal to BCD Priority Encoder on Bread Board using 74147 IC.

### Task # 03

Using the output from the above task light up two seven segment displays.



